

# Experiment 5

Date: 14/12/2022

## *Title:* Wheatstone Bridge

Submitted to

(Romina Group 6)

*Department  
of*

*Basic Sciences and Humanities*

*By*

*(Abdulahi Ogunlesi  
22114031)*

-----  
-----  
-----  
-----  
-----

**In partial fulfillment of the requirements for the course**

## ***PHY 102***

### **Content of report**


#### **➤ Aim of experiment**

1. To determine the resistance of the unknown resistor
2. To study and understand the usage of wheatstone bridge in determining the resistance of an unknown resistor

#### **➤ Apparatus**

1. Power supply (3v)
2. Resistors(2x)
3. Connecting cable
4. Multimeter
5. Galvanometer
6. Wheatstone bridge

#### **➤ Diagram**

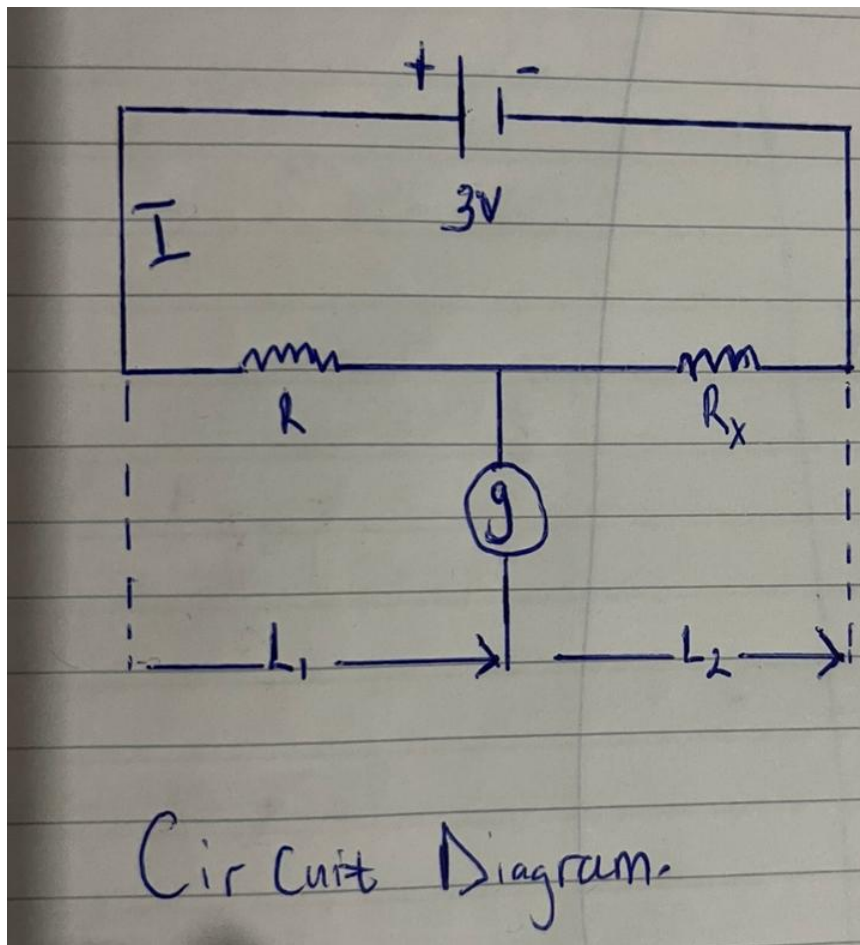

### ➤ Procedure

1. The circuit was set up
2. The value of the current was found with the multimeter
3. The resistance of the known resistor was measured
4.  $L_1$  was recorded on the galvanometer when the multimeter showed zero
5. The resistance of the unknown resistor was found ( $R_x$ )

### ➤ Equation

$$R_x/L_2 = R/L_1$$

$$R_x = R * L_2 / L_1$$

$$L_1 + L_2 = 100$$

$$L_1 = 100 - L_2$$

Where  $R_x$  = unknown resistor ( $\Omega$ )

$R$  = known resistor

$L_2$  = measured length (cm)

$L_1$  = calculated length (cm)

### ➤ Table

$L_1$ (cm)	$L_2$ (cm)	$R_{\Omega}$	Measured value $R_x$	Calculated value $R_x$
18.70	81.30	21.70	98.70	94.34

### ➤ Graph (*where applicable*)

***There is no graph for this experiment***

### ➤ Calculations

$$L_1 + L_2 = 100$$

$$L_1 = 100 - L_2$$

$$100 - 81.30 = 18.70 \text{ cm}$$

$$R_x / L_2 = R / L_1$$

$$R_x = R * L_2 / L_1$$

$$= 21.70 * 81.30 / 18.70$$

$$= 94.34 (\Omega)$$

### ➤ Results & Discussion

The Calculated value of  $R_x$  is not equal to the measured value of  $R_x$  because there must have been some errors in the during the experiment in lab(errors like parallax errors, malfunction of the lab apparatus)

The percentage error of the  $R_x = \text{Actual value} - \text{Expected value} / \text{Expected value} * 100$   
 $= 98.70 - 94.34 / 94.34 * 100$   
 $= 4.62\% \text{ error}$

#### ➤ Conclusion

The experiment was successful and the resistance of the unknown resistor was determined with the usage of wheatstone bridge.