

Experiment 1-Ohm's Law

Date: 19/10/2022

Title: Ohm's Law

Submitted to

(Ernest Mbelu)

***Department
of***

Basic Sciences and Humanities


By

***(Abdulahi Ogunlesi
22114031)***

In partial fulfillment of the requirements for the course
PHY 102

Content of report

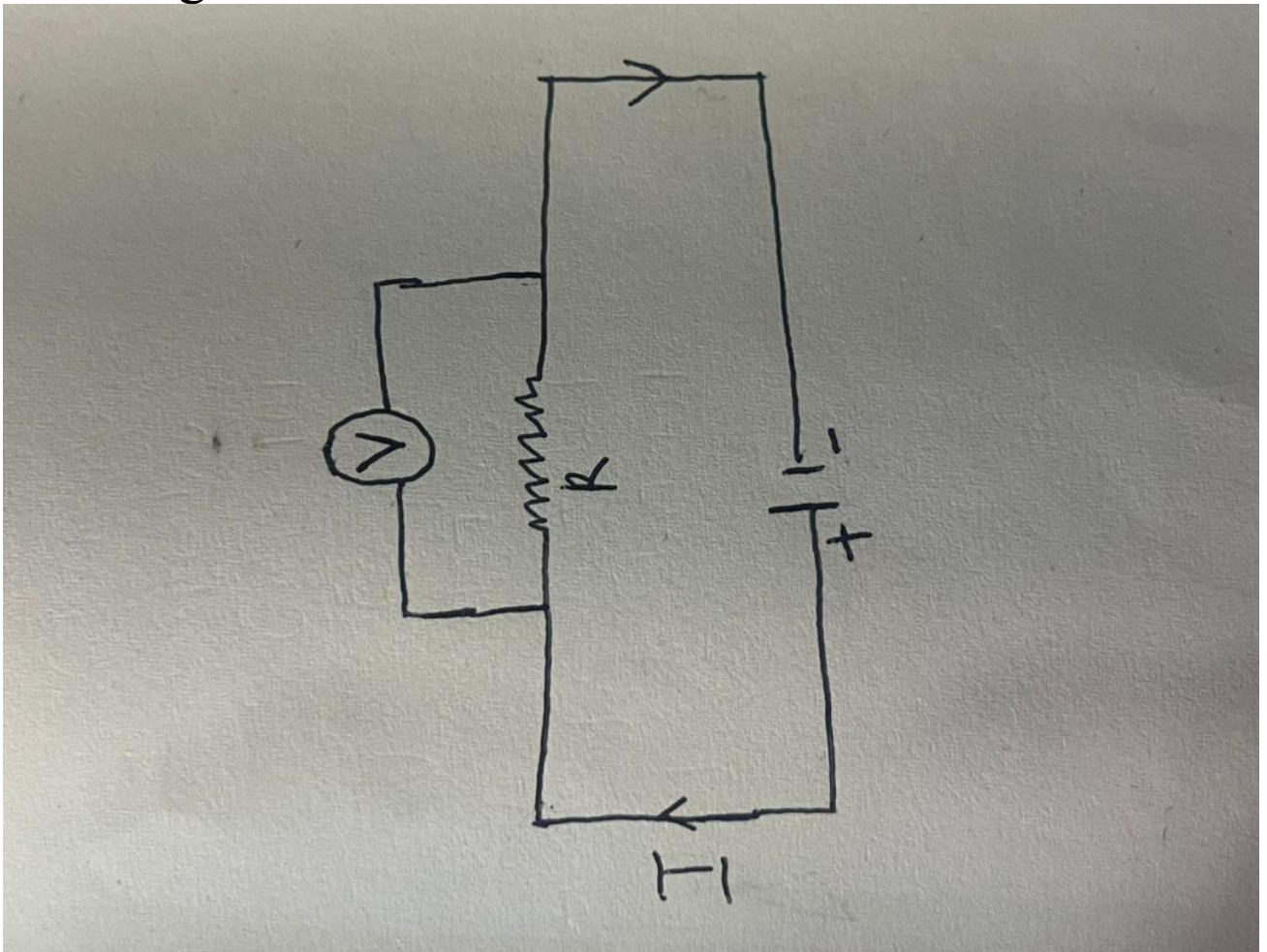- Aim of experiment: Confirmation of Ohm's law
- Apparatus
 1. Connecting cables
 2. Resistor
 3. Power supply
 4. Digital multimeter
- Diagram



➤ Procedure

1. Get your measured resistance(9.88)
2. Determine the resistance of each resistors
3. Adjust the voltage of the power supply to a suitable value and keep it constant
4. Measure the current and voltage
5. Repeat the third step for other resistors


➤ Equation: $R=V/I$

➤ Table

Measured resistance = 9.88

Ref(V ₁ V)	V _(v)	I _(mA)	R(Ω)
5	3.90	0.39	10
10	8.93	0.90	9.92
15	14.56	1.47	9.90
20	19.95	2.03	9.83

➤ Graph

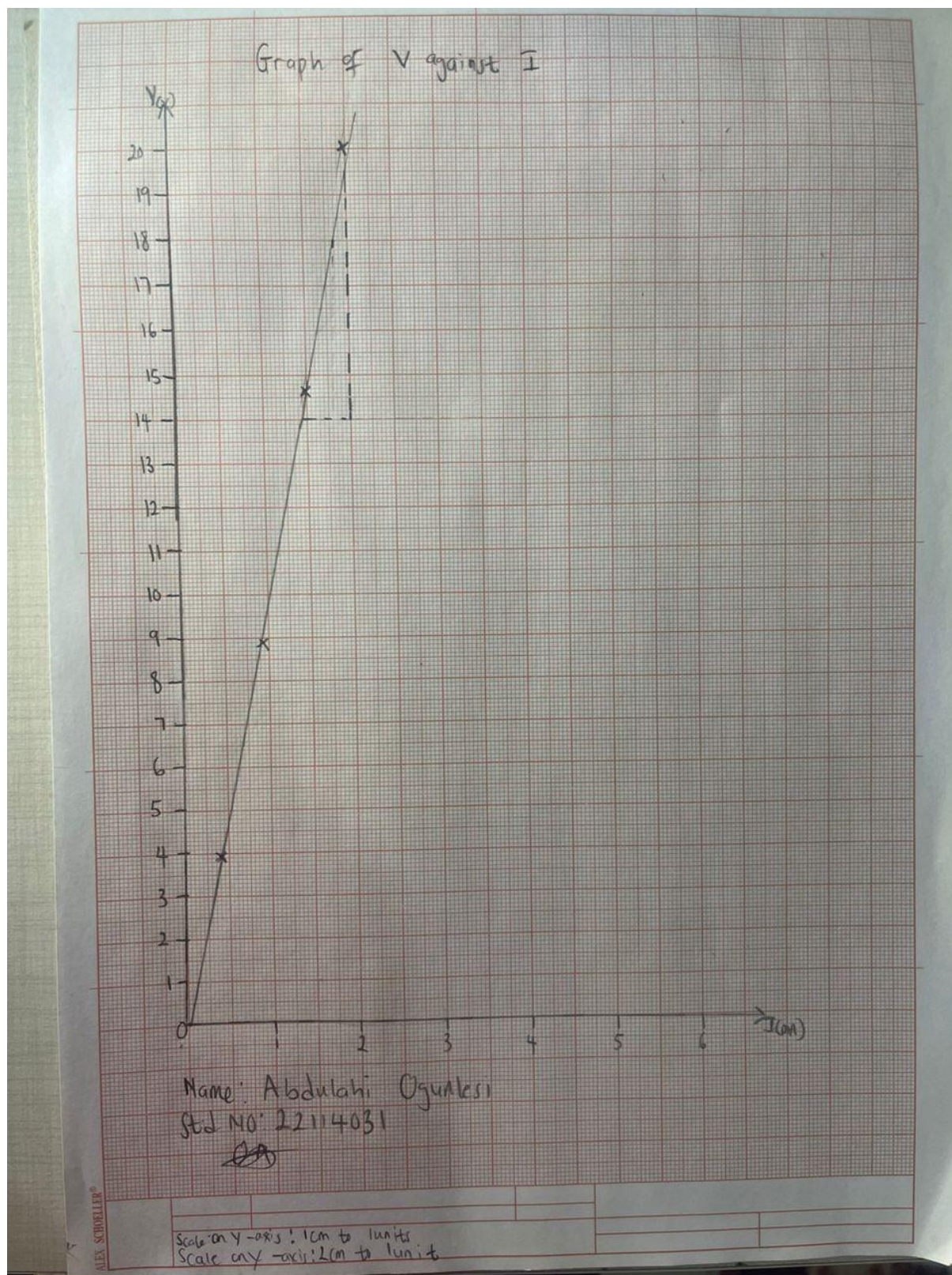

➤ Calculations

$$\begin{aligned}\text{Slope}(R) &= y_2 - y_1 / x_2 - x_1 \\ &= 19.5 - 14 / 2 - 1.4 \\ &= 5.5 / 0.6 \\ &= 9.19 \text{ k}\Omega\end{aligned}$$

➤ Results & Discussion

Resistance is the slope of the voltage against current graph.

➤ Conclusion

The experiment is about ohm's law. The values of R are closed which means ohm's law is confirmed.